

SUBTRACTOR & RIPPLE CARRY ADDER & CARRY LOOKAHEAD ADDER

Presented by Nabanita Das



HALF SUBTRACTOR

❑ Subtracting a single-bit binary value Y from X (i.e. $A - B$) produces a difference bit D and a borrow out bit B-out.

❑ This operation is called half subtraction and the circuit to realize it is called a half subtractor.

Half Subtractor Truth Table:

Inputs		Outputs	
A	B	D	B-out
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

  

$$D(A,B) = \Sigma (1,2)$$

$$D = A'B + AB'$$

$$D = A \oplus B$$

$$B\text{-out}(A, B) = \Sigma (1)$$

$$B\text{-out} = A'B$$

FULL SUBTRACTOR

□ Subtracting two single-bit binary values, Y, B-in from a single-bit value X produces a difference bit D and a borrow out B-out bit. This is called full subtraction.

Truth Table:

Inputs			Outputs	
X	Y	B-in	D	B-out
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$S(X, Y, B\text{-in}) = \Sigma (1, 2, 4, 7)$$

$$B\text{-out}(x, y, B\text{-in}) = \Sigma (1, 2, 3, 7)$$

Difference D

XY B-in		X			
		00	01	11	10
0		0	2 1	6	4 1
1		1 1	3	7 1	5

Y

$$D = X'Y'(B\text{-in}) + X'Y(B\text{-in})' + XY'(B\text{-in})' + XY(B\text{-in})$$

$$D = X \oplus Y \oplus (B\text{-in})$$

Borrow B-out

XY B-in		X			
		00	01	11	10
0		0	2 1	6	4
1		1 1	3 1	7 1	5

Y

B-out = $X'Y + X'(B\text{-in}) + Y(B\text{-in})$

FULL SUBTRACTOR CIRCUIT

$$D = X \oplus Y \oplus (B\text{-in})$$

$$B\text{-out} = X'Y + X'(B\text{-in}) + Y(B\text{-in})$$


$$D = X'Y'Bin + X'YBin' + XY'Bin' + XYBin$$

$$= (X'Y' + XY)Bin + (X'Y + XY')Bin'$$

$$= (X \oplus Y)'Bin + (X \oplus Y)Bin'$$

$$= X \oplus Y \oplus Bin$$

$$Bout = X'.Y + X'.Bin + Y.Bin$$

 

RIPPLE CARRY ADDER

- An n-bit adder used to add two n-bit binary numbers can be built by connecting in series n full adders.
 - Each full adder represents a bit position j (from 0 to $n-1$).
 - Each carry out C_{out} from a full adder at position j is connected to the carry in C_{in} of the full adder at the higher position $j+1$.
 - In parallel adder circuits, the carry output of one stage serves as the carry input of the succeeding stage, thus being called the 'ripple' carry adder.

Ripple'? Why called so?

What happens when we throw a stone in the water? The water around the stone-hit area flows ahead in the form of ripples. Similarly, in the Ripple Carry Adder, the Carry bit 'ripples' forward into the system.


MATHEMATICALLY WHEN WE ADD TWO NUMBERS-

Consider two 4-bit binary numbers $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$ are to be added.

Mathematically, the two numbers will be added as-

From here, we have-

$$C_1 = C_0$$

 

RIPPLE CARRY ADDER

In Ripple Carry Adder,


Each full adder has to wait for its carry-in from its previous stage full adder.

Thus, nth full adder has to wait until all (n-1) full adders have completed their operations.

This causes a delay and makes ripple carry adder extremely slow.

The situation becomes worst when the value of n becomes very large.

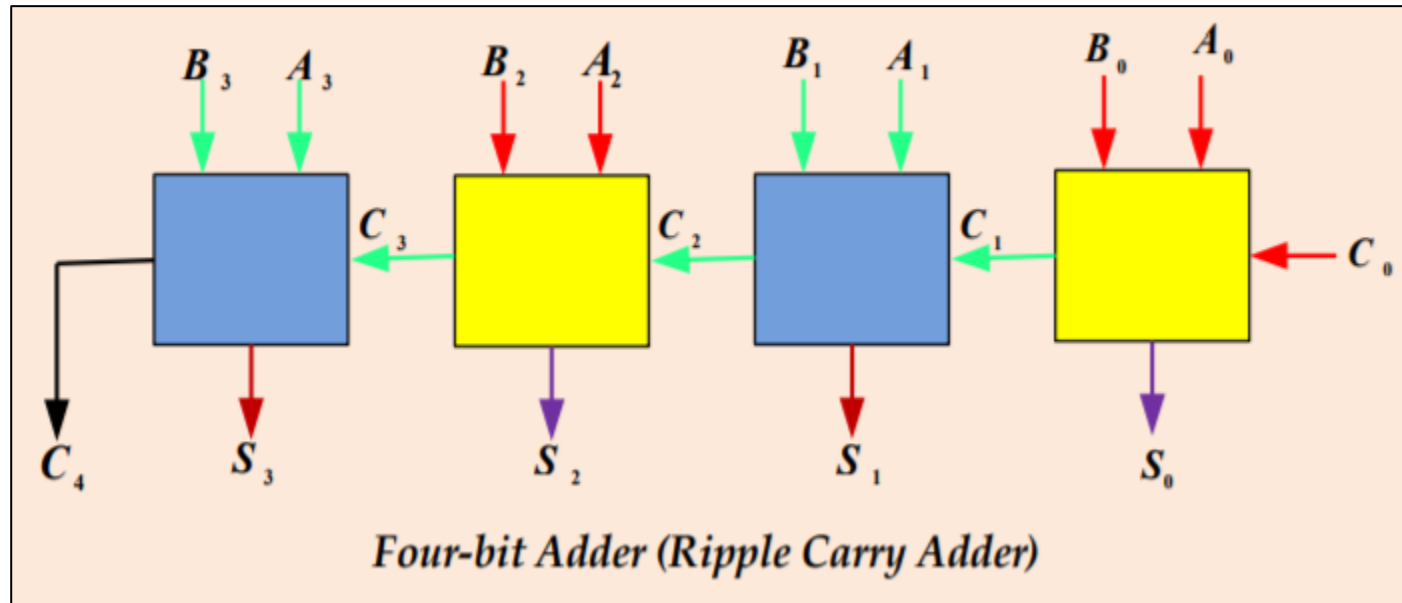To overcome this disadvantage, Carry Look Ahead Adder comes into play.



CARRY LOOKAHEAD ADDER

A look ahead carry adder is fast adder which improves speed by reducing the amount of time required to determine carry bits. It reduces the time which are delayed at each stage.

Let us consider a full adder. We have the inputs signals A, B, and Cin. If we consider the addition of these three variables in every possible case, we get a truth table like the one below.

INPUT OUTPUT						
Row	A	B	Cin	Sum	Cout	
0	0	0	0	0	0	No carry generation C _{out} =0
1	0	0	1	1	0	
2	0	1	0	1	0	Carry propagation C _{out} = C _{in}
3	0	1	1	0	1	
4	1	0	0	1	0	
5	1	0	1	0	1	
6	1	1	0	0	1	Carry generation C _{out} = 1
7	1	1	1	1	1	

EXPRESSION FOR CARRY GENERATION & PROPAGATION

From truth table , carry generation in row 6th and 7th is given by:-

$$G_i = A_i B_i$$

Similarly the carry propagation P_i occur with either $A_i = 1$ and $B_i = 0$ or vice versa.

$$P_i = A_i \oplus B_i$$

G_i is known as the carry Generate signal

P_i is known as the carry propagate signal

The full adder circuit we will give two outputs named as Sum, Carry out.

$$S = A \oplus B \oplus (C\text{-in})$$

$$C\text{-out} = (A \oplus B) (C\text{in}) + AB$$

The new expressions for the output sum and the carryout are given by:-

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$


MATHEMATICALLY WHEN WE ADD TWO NUMBERS-

Consider two 4-bit binary numbers $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$ are to be added.

Mathematically, the two numbers will be added as-

From here, we have-

$$C_1 = C_0$$

 

CONTD.

$$\text{Sum} = P_i \oplus C_i$$

$$\text{Carry} = G_i + P_i \cdot C_i$$


We can calculate the output carry C_1 , C_2 , C_3 , and C_4 using the above derived equations as:

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$
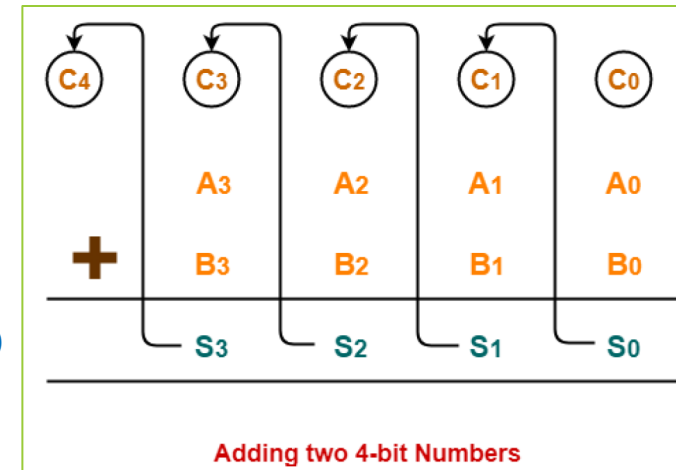
$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$




IMPLEMENTATION OF CARRY GENERATOR CIRCUITS-

Implementation Of C1-

The carry generator circuit for C1 is implemented as shown below.

It requires 1 AND gate and 1 OR gate.

$$C_1 = C_0P_0 + G_0$$

 


Similarly, implementation Of C2-

The carry generator circuit for C2 is implemented as shown below.

It requires 2 AND gates and 1 OR gate.

$$C_2 = C_0P_0P_1 + G_0P_1 + G_1$$

 

4 BIT CARRY LOOKAHEAD ADDER CIRCUIT

