



K-MAP WITH DON'T CARE CONDITIONS

Presented by Nabanita Das

DON'T CARE CONDITIONS

- Real circuits don't always need to have an output defined for every possible input.
- The “**Don't Care**” conditions allow us to replace the empty cell of a **K-Map** to form a grouping of the variables.
- In a K-map, a don't care condition is identified by an *X* in the cell of the minterm (s) for the don't care inputs, as shown below.
- In performing the simplification, we can consider a “**Don't Care**” cell as either 1 or 0 or ignore the *X*'s when creating our groups.

WX \ YZ	YZ			
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

Don't Care Conditions

Don't care conditions are part of function specification.

$$f = \sum m(\dots) + \sum d(\dots)$$

$$f = \prod M(\dots) \prod D(\dots)$$

They can be used for both sum-of-product and product-of-sum forms of functions.

DON'T CARE CONDITIONS

- Consider this example. In one grouping in the K-map below, we have the function:

$$F(W, X, Y, Z) = W'X' + YZ$$

$$F(W, X, Y, Z) = W'Z + YZ$$

- A different grouping gives us the function:
- However, the values for which they differ, are the inputs for which we have don't care conditions.
- Two possible solutions , both are acceptable.

WX \ YZ	YZ			
	00	01	11	10
00	×	1	1	×
01		×	1	
11	×		1	
10			1	

WX \ YZ	YZ			
	00	01	11	10
00	×	1	1	×
01		×	1	
11	×		1	
10			1	

SOLVED EXAMPLE OF DON'T CARE CONDITIONS

$$F(A, B, C) = \sum m(1, 3, 7) + \sum d(0, 5)$$

Circle the x's that help get bigger groups of 1's (or 0's if POS).

Don't circle the x's that don't help.

		BC			
		00	01	11	10
A	0	⁰ X	¹ 1	³ 1	²
	1	⁴	⁵ X	⁷ 1	⁶

Reduced form : $F = C$

Solved example of Don't Care Conditions

$$F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$$

		C				
		CD				
A	AB	00	01	11	10	B
	00	X	1	1	X	
	01	0	X	1	0	
	11	0	0	1	0	
	10	0	0	1	0	
		D				

(a) $F = CD + \overline{A} \overline{B}$

		C				
		CD				
A	AB	00	01	11	10	B
	00	X	1	1	X	
	01	0	X	1	0	
	11	0	0	1	0	
	10	0	0	1	0	
		D				

(b) $F = CD + \overline{A} D$

Two possible solutions , both are acceptable.

Solved example of Don't Care Conditions

$$F(A, B, C, D) = \sum m(1, 3, 5, 7, 9) + \sum d(6, 12, 13)$$

		CD			
		00	01	11	10
AB	00	0	1	1	0
	01		1	1	x
	11	x	x	0	0
	10	0	1	0	0

Reduced Form $F = A'D + C'D$

Another Solved example of Don't Care Conditions Using Maxterm

$$f(A,B,C,D) = \prod m(1,6,10,11,12,13,15) + \prod d(4,5,7,8,14)$$

		CD			
		00	01	11	10
AB	00		0		
	01	x	x	x	0
	11	0	0	0	x
	10	x		0	0

$$F = (A + C + D') (B') (A' + C')$$

MINIMIZE THE FOLLOWING FUNCTION IN SOP MINIMAL FORM

- $F(A, B, C, D) = m(1, 2, 6, 7, 8, 13, 14, 15) + d(3, 5, 12)$

$$f = AC'D' + A'D + A'C + AB$$

		CD			
		00	01	11	10
AB	00		1	X	1
	01		X	1	1
	11	X	1	1	1
	10	1			

MINIMIZE THE FOLLOWING FUNCTION IN POS MINIMAL FORM

$$F(A,B,C,D) = M(6,7,8,9) + d(10,11,12,13,14,15)$$

So, the minimized POS form of the function is:

$$F = A'(B' + C')$$

CD		00	01	11	10
AB	00				
	01			0	0
	11	X	X	X	X
	10	0	0	X	X

SOME PROBLEMS

1. $F(A, B, C, D) = \pi M(0, 2, 3, 6, 7) + \pi d(8, 10, 11, 15)$
2. $F(A, B, C, D) = \Sigma m(1, 2, 3, 5, 6, 11, 12) + \Sigma d(7, 8, 10, 14)$
3. $F(W, X, Y, Z) = \Sigma m(2, 3, 7, 11, 12, 13, 14, 15) + \Sigma d(0, 4, 6, 8, 10)$
4. $F(A, B, C, D) = \pi M(1, 3, 5, 7) + \pi d(9, 10, 11)$