



# *ENCODER*

*Presented by*


*Nabanita Das*

*Assistant Professor, Department of CSE & IT*

---
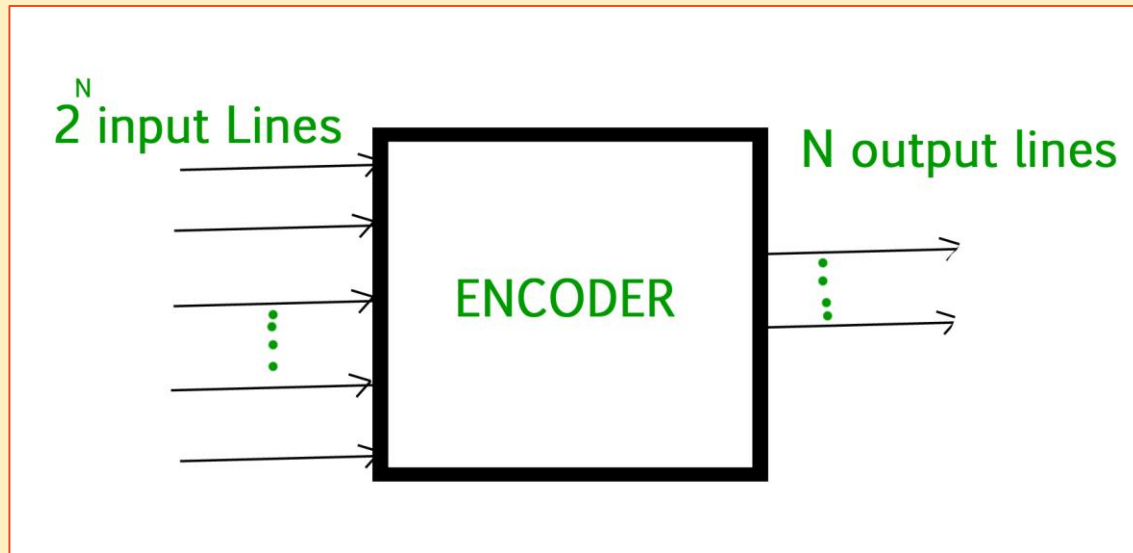
# ENCODER

- An Encoder is a combinational logic circuit. It performs the inverse operation of Decoder.
- An Encoder converts an active input signal into a coded output signal.
- It has ' $2^N$ ' inputs and 'N' outputs.
- An Encoder has ' $2^N$ ' input lines, only one of which is activated at a given time, and produces an N-bit output code, depending on which input is activated.



INPUTS				OUTPUTS	
$D_0$	$D_1$	$D_2$	$D_3$	A	B
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

# ENCODER


- Encoders are used to translate the rotary or linear motion into a digital signal. Rotary encoders are a type of sensor that measures the rotation of a mechanical shaft.
- The difference between Decoder and Encoder is that Decoder has Binary Code as an input while Encoder has Binary Code as an output.
- Encoder is an Electronics device that converts the analog signal to digital signal such as BCD Code.
- The most common technique to change an analog signal to digital data is called pulse code modulation (PCM). A PCM encoder has the following three processes:
  - a.Sampling
  - b.Quantization
  - c.Encoding

## Types of Encoders

- i. Priority Encoder
  - ii. Decimal to BCD Encoder
  - iii. Octal to Binary Encoder
  - iv. Hexadecimal to Binary Encoder
-
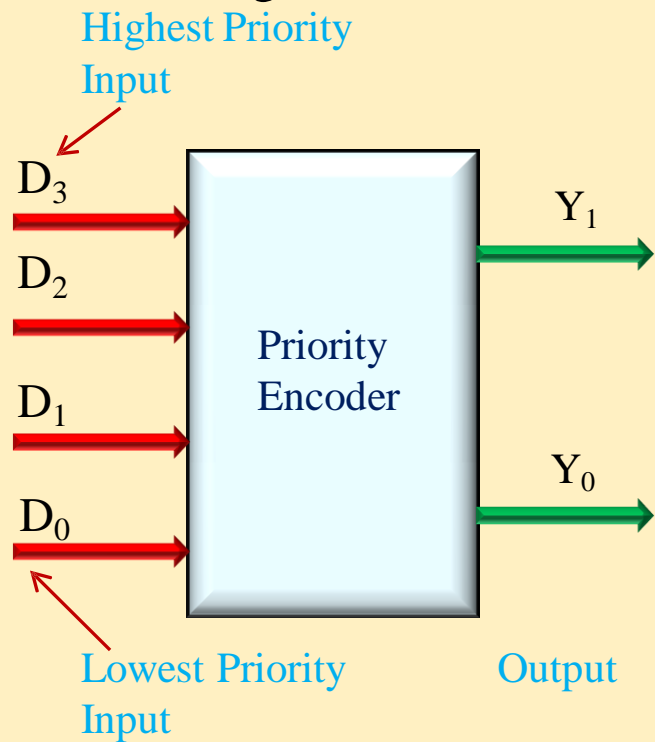
# PRIORITY ENCODER:

- As the name indicates, the priority is given to inputs line.
- If two or more input lines are high at the same time i.e 1 at the same time, then the input line with high priority shall be considered.
- Block diagram and Truth table of Priority Encoder are shown below.



*Block Diagram of Priority Encoder*

TRUTH TABLE:

INPUTS				OUTPUTS		V
$D_3$	$D_2$	$D_1$	$D_0$	$Y_1$	$Y_0$	
0	0	0	0	x	x	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

- There are four inputs  $D_0, D_1, D_2, D_3$  and two outputs  $Y_1$  and  $Y_2$ .
- $D_3$  has highest priority and  $D_0$  is at lowest priority.
- If  $D_3=1$  irrespective of other inputs then output  $Y_1 Y_0=11$ .
- $D_3$  is at highest priority so other inputs are considered as don't care.

### K-map for $Y_1$ and $Y_0$

$D_1 D_0$ $D_3 D_2$		$D_1 D_0$			
		00	01	11	10
00	X	0	0	0	0
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1


$D_1 D_0$ $D_3 D_2$		$D_1 D_0$			
		00	01	11	10
00	X	0	1	1	1
01	0	0	0	0	0
11	1	1	1	1	1
10	1	1	1	1	1

$$Y_1 = D_2 + D_3$$

$$Y_0 = D_3 + \overline{D_2} D_1$$

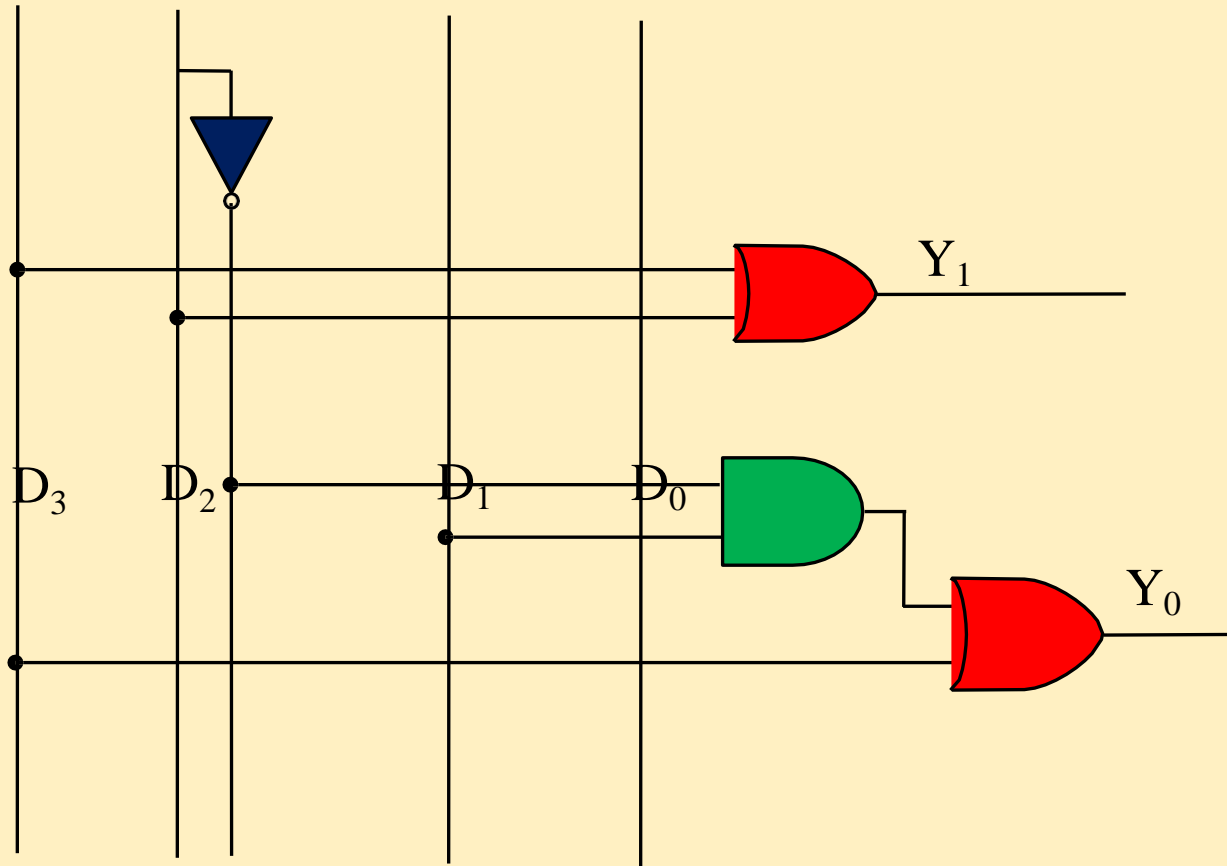
# LOGIC DIAGRAM OF PRIORITY ENCODER

$$Y_1 = D_2 + D_3$$
$$Y_0 = D_3 + \overline{D_2} D_1$$


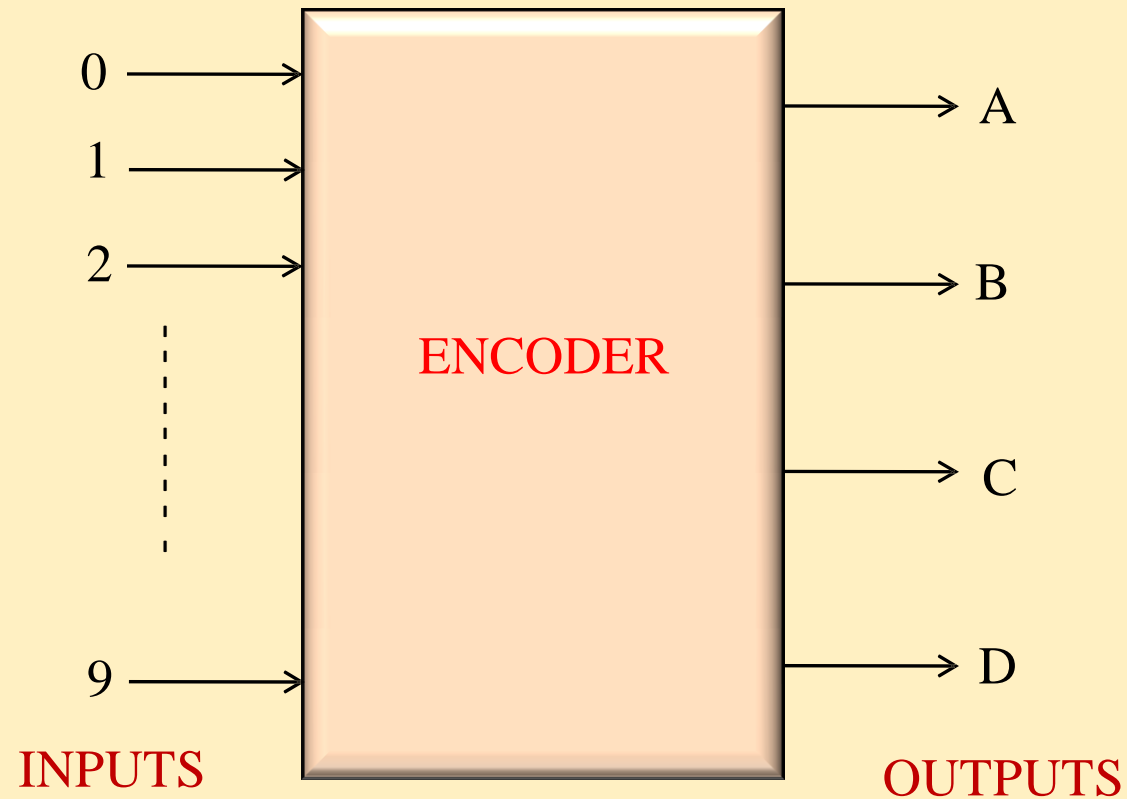
# *DECIMAL TO BCD ENCODER*

It has ten inputs corresponding to ten decimal digits (from 0 to 9) and four outputs (A,B,C,D) representing the BCD.




# Truth table

INPUTS										BCD OUTPUTS			
0	1	2	3	4	5	6	7	8	9	A	B	C	D
1	0	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	0	0	0	1	0	0
0	0	0	0	0	1	0	0	0	0	0	1	0	1
0	0	0	0	0	0	1	0	0	0	0	1	1	0
0	0	0	0	0	0	0	1	0	0	0	1	1	1
0	0	0	0	0	0	0	0	1	0	1	0	0	0
0	0	0	0	0	0	0	0	0	1	1	0	0	1



- From Truth Table it is clear that the output A is HIGH when input is 8 OR 9 is HIGH  
Therefore  $A=8+9$
  - The output B is HIGH when 4 OR 5 OR 6 OR 7 is HIGH Therefore  
 $B=4+5+6+7$
  - The output C is HIGH when 2 OR 3 OR 6 OR 7 is HIGH  
Therefore  $C=2+3+6+7$
  - Similarly  $D=1+3+5+7+9$
-


# DECIMAL TO BCD ENCODER

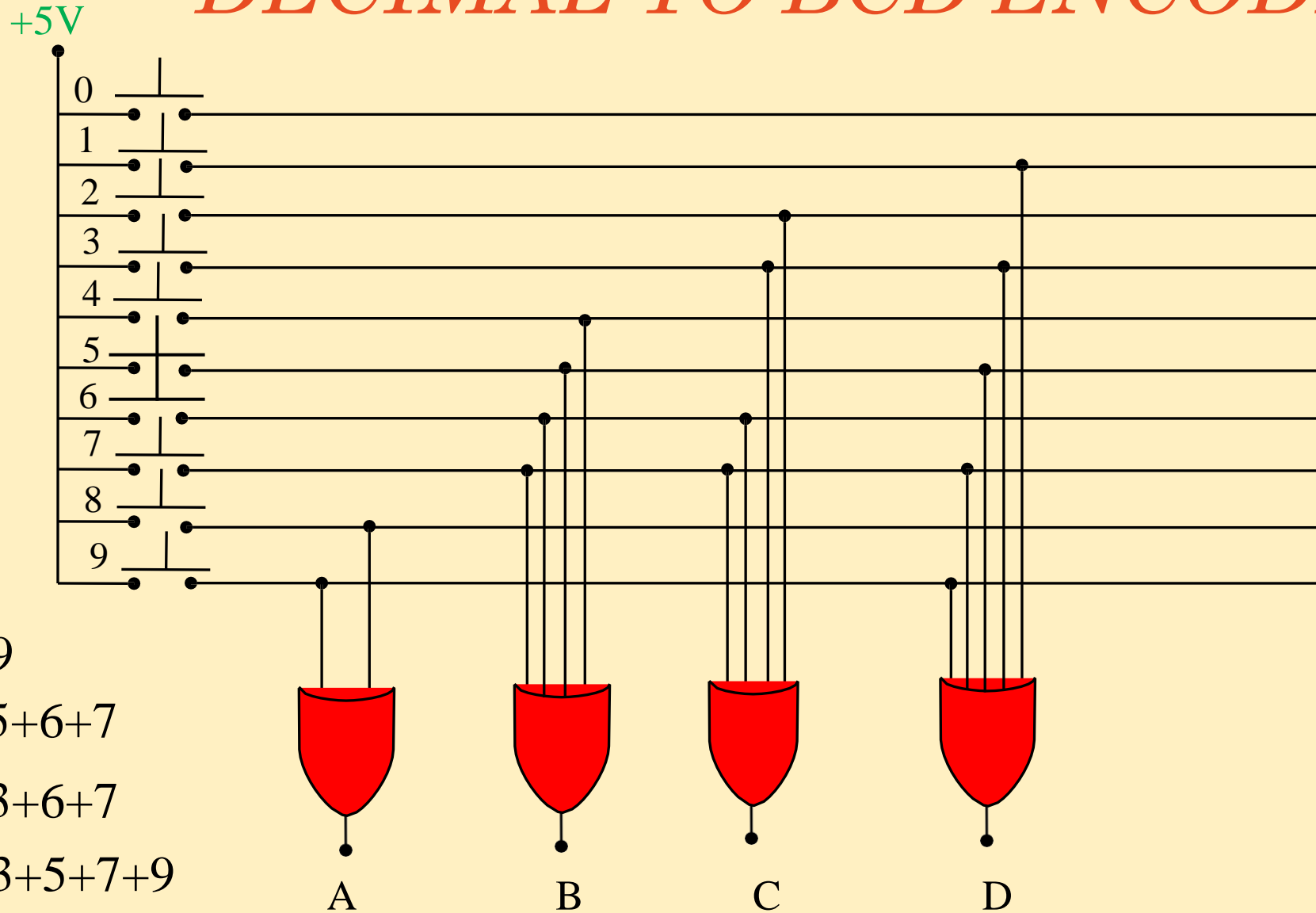

- $A = 8 + 9$
- $B = 4 + 5 + 6 + 7$
- $C = 2 + 3 + 6 + 7$
- $D = 1 + 3 + 5 + 7 + 9$
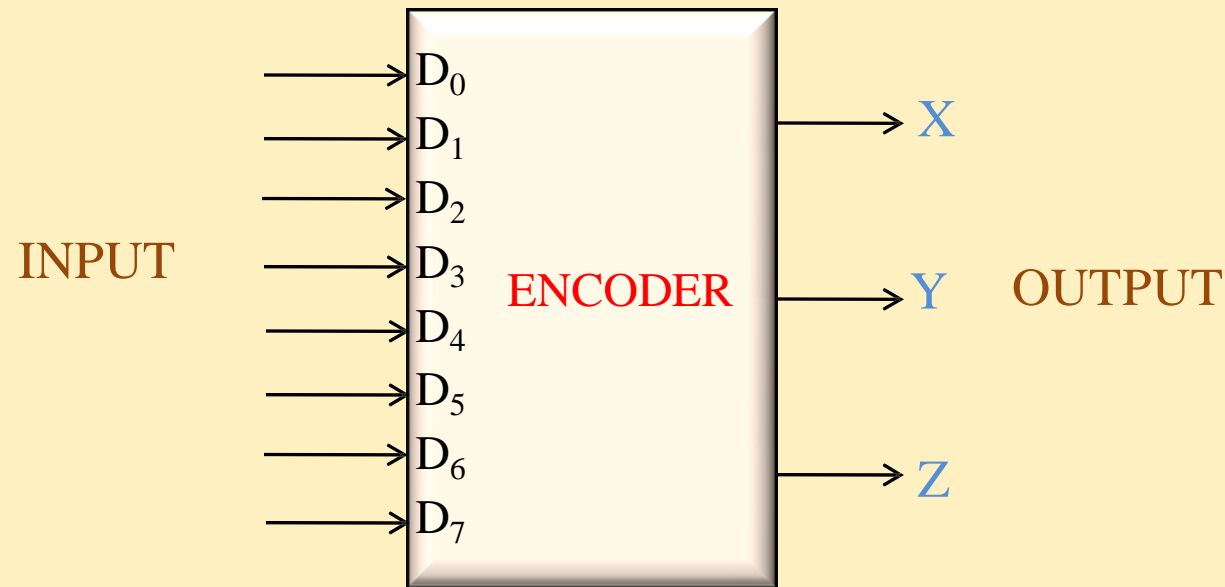
# *OCTAL TO BINARY ENCODER*

- It has eight inputs and three outputs.
- Only one input has one value at any given time.
- Each input corresponds to each octal digit and output generates corresponding Binary Code.



# TRUTH TABLE

INPUT								OUTPUT		
D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	X	Y	Z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

## *From Truth table*

$$X = D_4 + D_5 + D_6 + D_7$$

$$Y = D_2 + D_3 + D_6 + D_7$$

$$Z = D_1 + D_3 + D_5 + D_7$$

- It is assumed that only one input is HIGH at any given time. If two outputs are HIGH then undefined output will be produced. For example  $D_3$  and  $D_6$  are HIGH, then output of Encoder will be 111. This output neither equivalent code corresponding to  $D_3$  nor to  $D_6$ .
  - To overcome this problem, priorities should be assigned to each input.
  - From the truth table it is clear that the output X becomes 1 if any of the digit  $D_4$  or  $D_5$  or  $D_6$  or  $D_7$  is 1.
  - $D_0$  is considered as don't care because it is not shown in expression.
  - If inputs are zero then output will be zero. Similarly if  $D_0$  is one, the output will be zero.
-

$$X = D_4 + D_5 + D_6 + D_7$$

$$Y = D_2 + D_3 + D_6 + D_7$$

$$Z = D_1 + D_3 + D_5 + D_7$$

### LOGIC DIAGRAM:

