



Flip-flop Conversion


Presented by Nabanita Das

FLIP FLOP CONVERSIONS

- SR to D
- SR to JK
- SR to T
- JK to T
- JK to D
- JK to SR
- D to T
- D to SR
- T to D

CONVERSION OF FLIP FLOPS

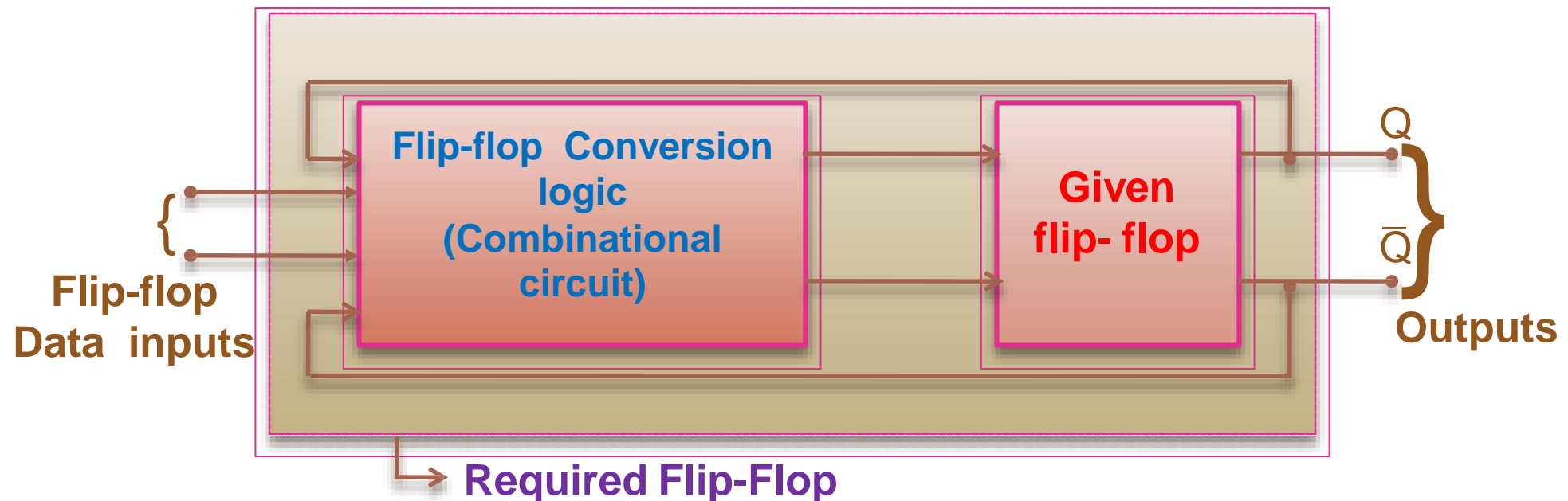The conversion from one type of flip flop to the other (say SR FF to JK FF) needs a systematic approach using the excitation tables and K map simplifications.



General model used to convert one type of FF to the other

PROCEDURE FOR CONVERSION

1. Draw the block diagram of the target flip flop from the given problem.
2. Write truth table for the target flip-flop.
3. Write excitation table for the available flip-flop.
4. Draw k-map for target flip-flop.
5. Draw the block diagram.

SR(Available) to D(Target) Flip flop Conversion

- Truth table of D Flip flop

Input	Present state	Next State
D	Q_n	Q_{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

Flip-flop inputs		Present output	Next output
S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

- Excitation table SR Flip Flop



Present state	Next state	Flip flop Inputs	
Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

SR to D Flip flop Conversion


Conversion Table

Input	Present state	Next state	Flip flop Inputs	
D	Q_n	Q_{n+1}	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

K- MAP SIMPLIFICATION

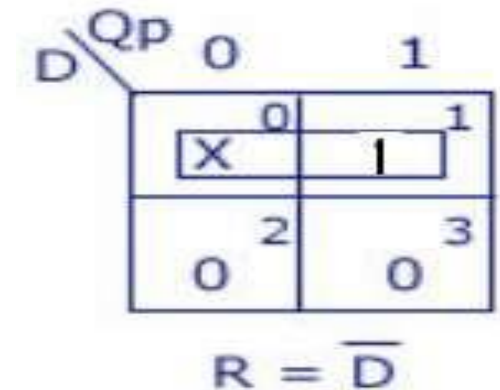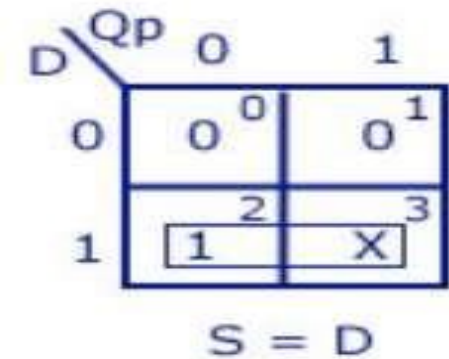

SR to D Flip Flop

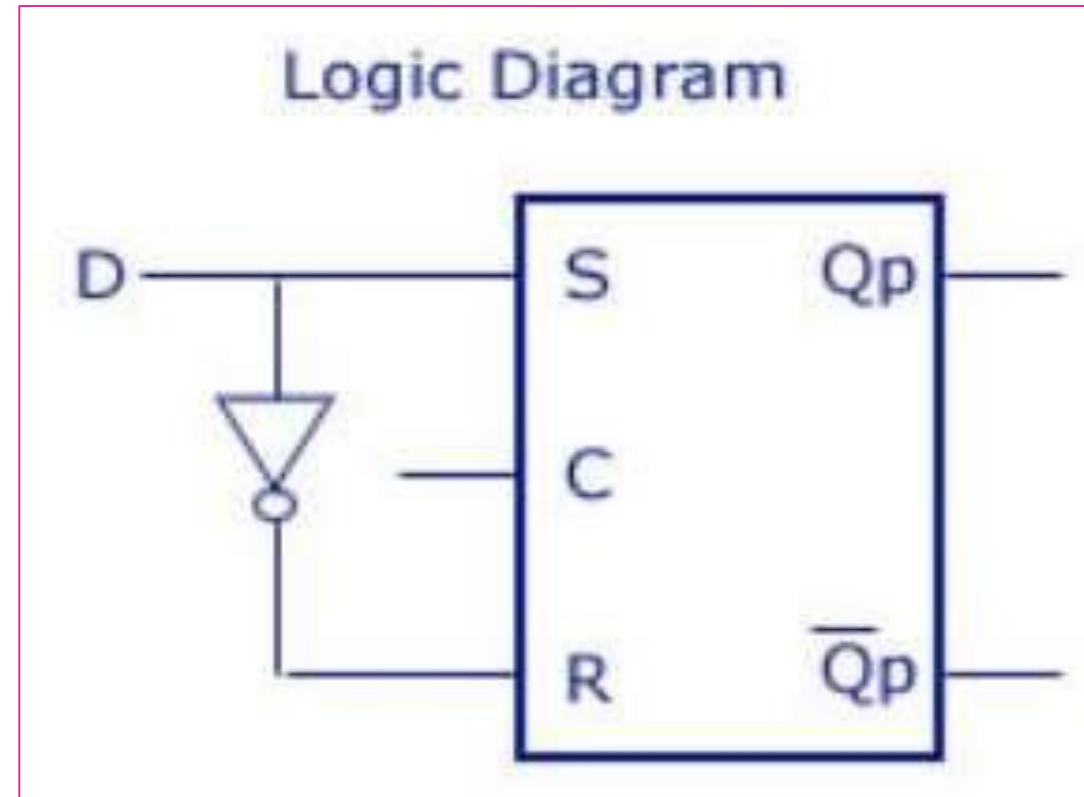

SR(Available) to JK(Target) Flip-Flop

- Truth table of JK Flip flop

Input		Present State	Next State
J	K	Q n	Qn+1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

- Excitation table SR Flip Flop

Present state	Next state	Flip flop Inputs	
Q n	Qn+1	S	R
0	0	0	X
1	0	0	1
0	1	1	0
1	1	X	0

Flip-flop inputs		Present output	Next output
S	R	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

SR(Available) to JK(Target) Flip-Flop

Conversion Table

Input		Present State	Next State	Flip-Flop Inputs	
J	K	Q _n	Q _{n+1}	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

SR to JK Flip- Flop

- K-map Simplification


J \ KQ _p	00	01	11	10
	0	1	3	2
0	0	X	0	0
1	1	X	0	1

$S = \bar{J}Q_p$

J \ KQ _p	00	01	11	10
	0	1	3	2
0	X	0	1	X
1	0	0	1	0

$R = KQ_p$

Logic Diagram (SR to JK)


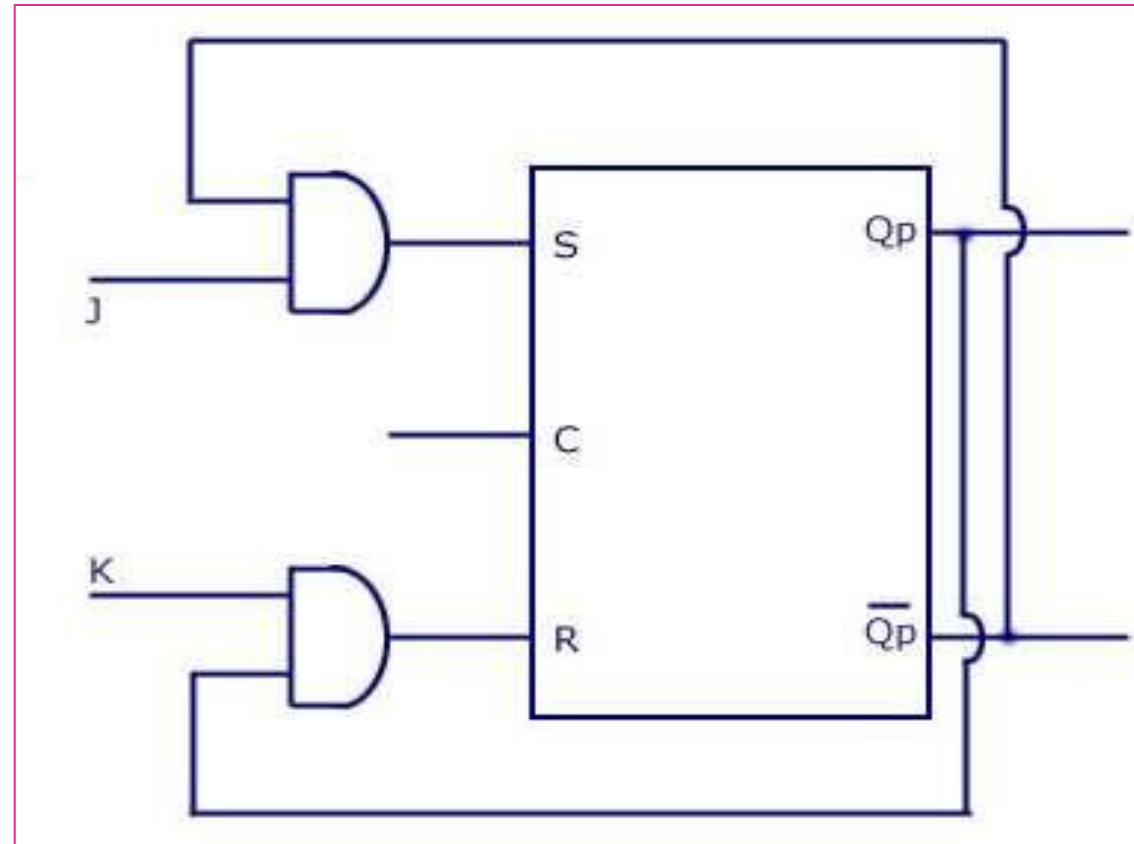


SR(Available) to T(Target) Flip Flop


K- MAP SIMPLIFICATION

Conversion Table

Input	Present state	Next state	Flip flop Inputs	
T	Q_n	Q_{n+1}	S	R
0	0	0	0	X
0	1	1	X	0
1	0	1	1	0
1	1	0	0	1

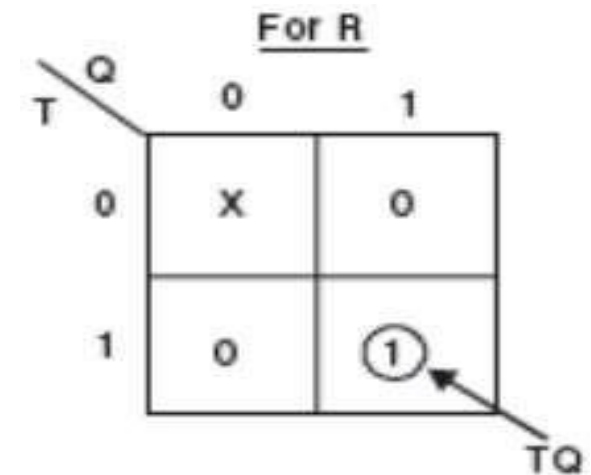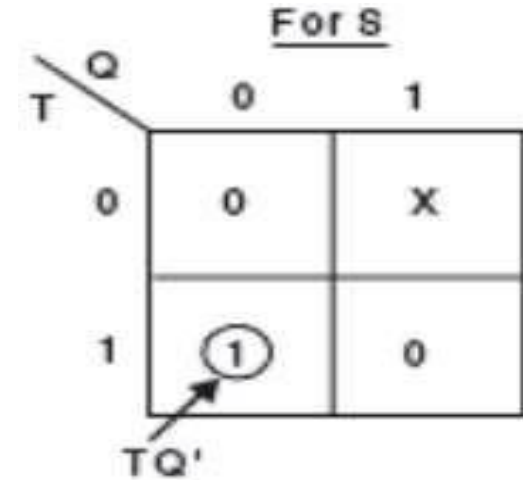

Logic Diagram (SR to T)

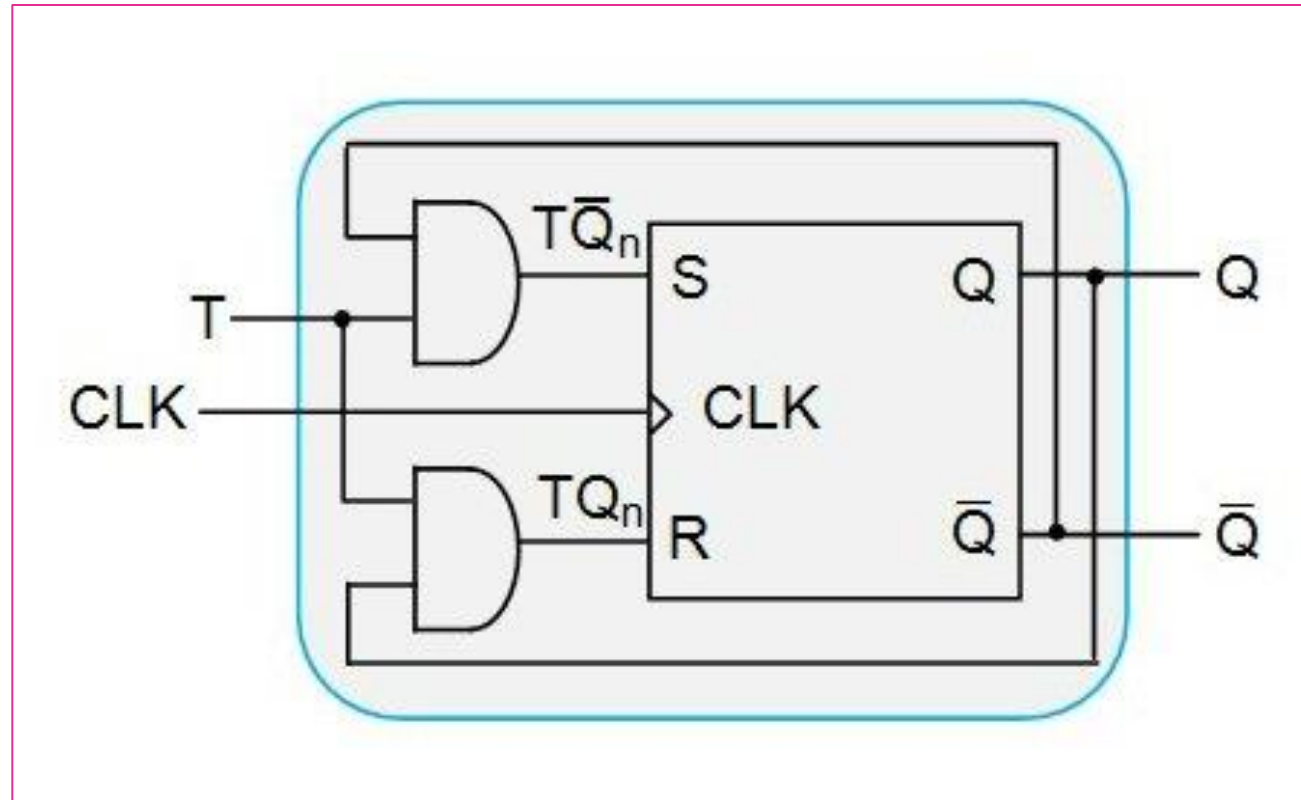

JK(Available) to T (Target) Flip-Flop

Input	Present state	Next state
T	Q n	Qn+1
0	0	0
0	1	1
1	0	1
1	1	0

Flip-flop inputs		Present output	Next output
J	K	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Excitation Table of JK Flip-Flop

Qn	Qn+1	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

JK(Available) to T (Target) Flip-Flop

Input	Present state	Next state	Flip flop Inputs	
T	Q_n	Q_{n+1}	J	K
0	0	0	0	X
0	1	1	X	0
1	0	1	1	x
1	1	0	x	1

K- MAP SIMPLIFICATION


T	Q_n	0	1
		0	1
0		0	X
1		2	3
		1	X

$$J=T$$

T	Q_n	0	1
		0	1
0		X	0
1		2	3
		X	1

$$K=T$$

Logic Diagram (JK to T) Flip- Flop

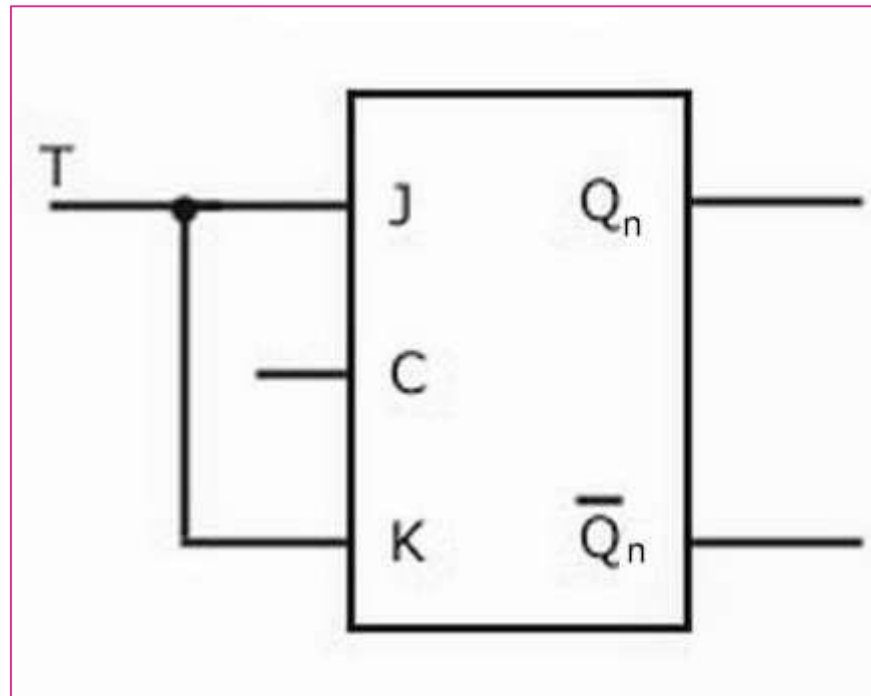

JK(Available) to D(Target)Flip-flop

Input	Present state	Next state
D	Q n	Qn+1
0	0	0
0	1	0
1	0	1
1	1	1

Flip-flop inputs		Present output	Next output
J	K	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Excitation Table of JK Flip-Flop



Qn	Qn+1	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

JK(Available) to D(Target) Flip-flop


Conversion Table

Input	Present state	Next state	Flip flop Inputs	
D	Q_n	Q_{n+1}	J	K
0	0	0	0	X
0	1	0	X	1
1	0	1	1	x
1	1	1	x	0

**K- MAP
SIMPLIFICATION**

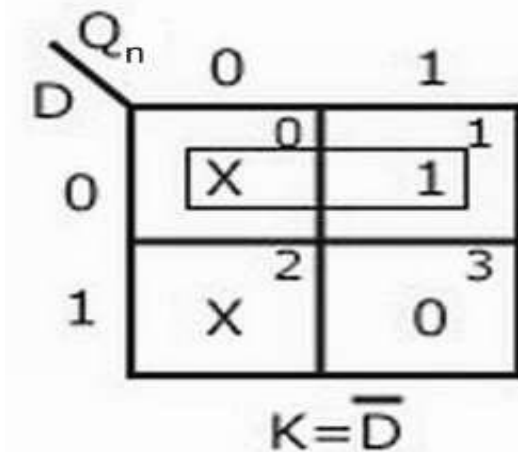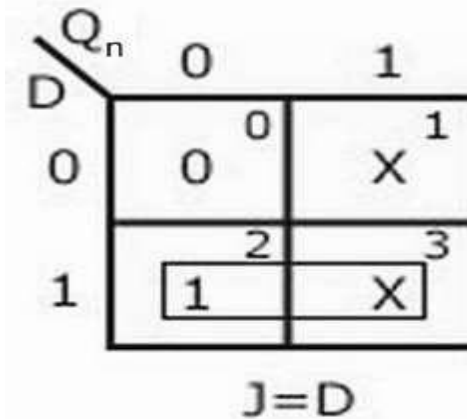

Logic Diagram (JK to D)

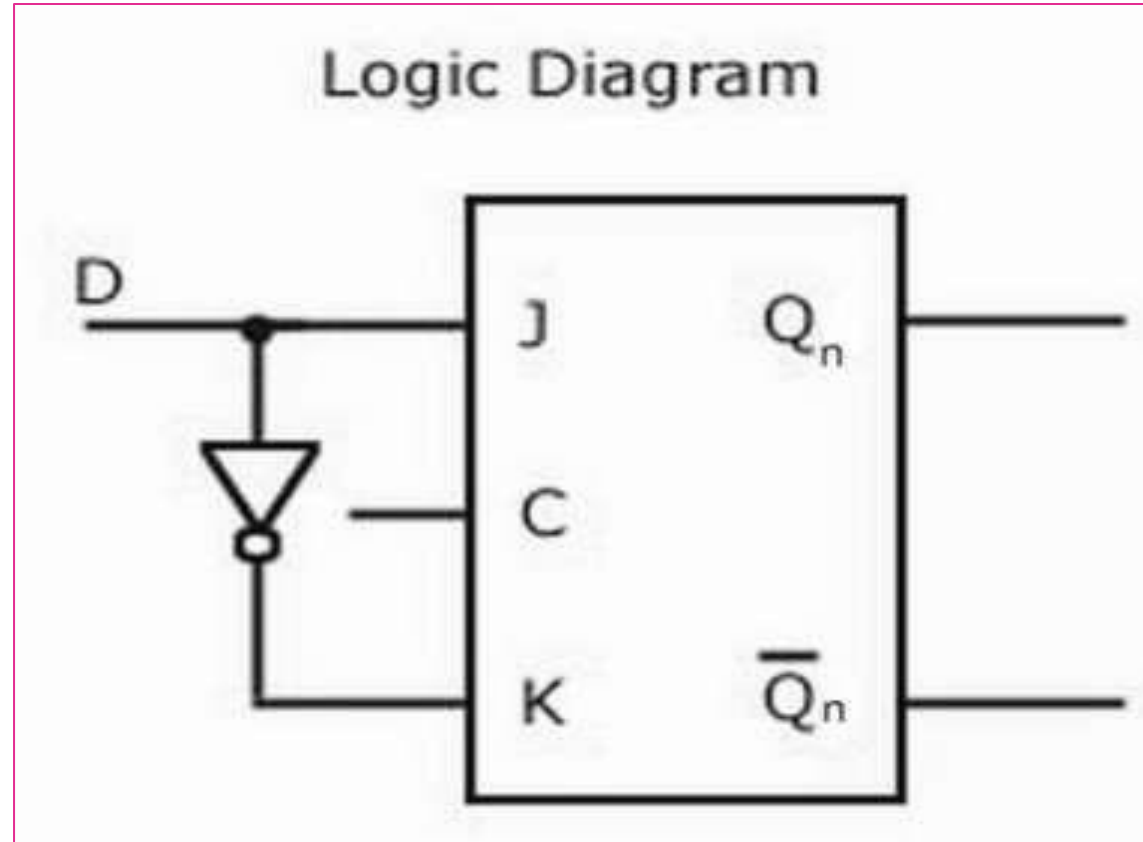

D(Available) to T(Target) Flip-Flop

Input	Present state	Next state
T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table of D Flip-Flop

Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

D(Available) to T(Target)Flip-Flop

Conversion Table

Input	Present State	Next state	Flip flop Inputs
T	Q n	Qn+1	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

**K- MAP
SIMPLIFICATION**


		Qn	
		0	1
T	0	0	1
	1	1	0

$$D = T'Q_n + TQ_n'$$

Logic Diagram(D to T) Flip-Flop Conversion

		Qn	
		0	1
T	0	0	1
	1	1	0

$$D = T'Q_n + TQ_n'$$

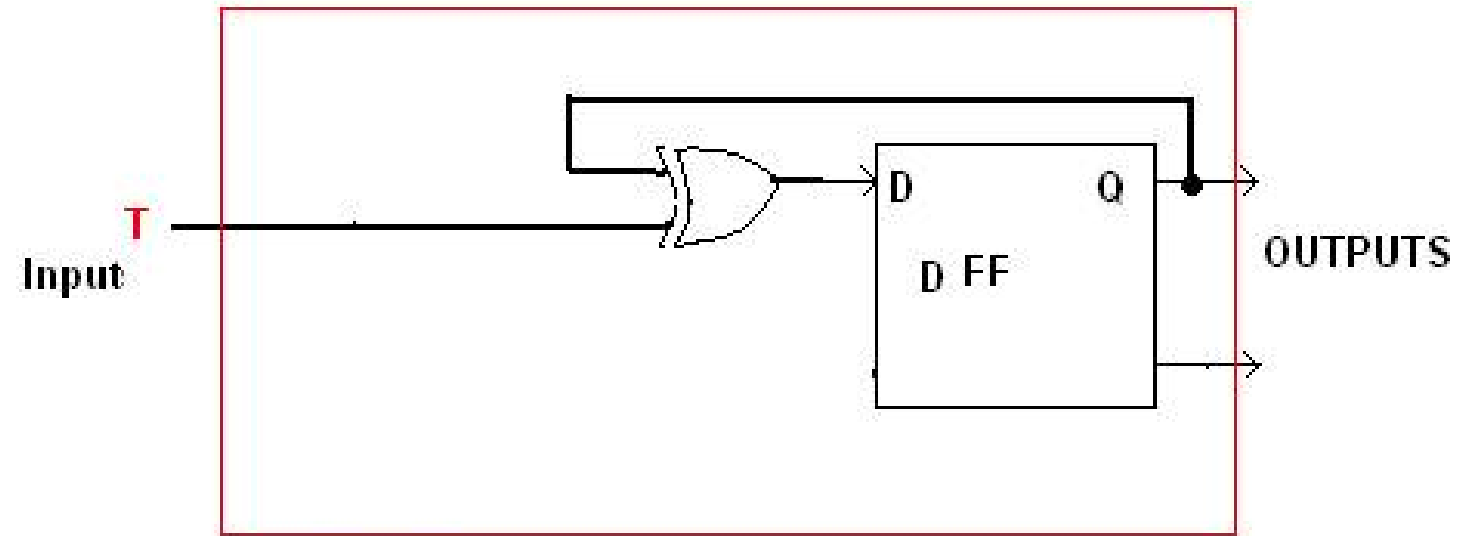

T (Available) to D(Target) Flip-Flop

Input	Present state	Next state
D	Q n	Qn+1
0	0	0
0	1	0
1	0	1
1	1	1

Excitation Table of T Flip-Flop

Q n	Qn+1	T
0	0	0
0	1	1
1	0	1
1	1	0

T (Available) to D(Target) Flip-flop

Conversion Table

Input	Present state	Next state	Flip flop Inputs
D	Q_n	Q_{n+1}	T
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

K- MAP SIMPLIFICATION


		Q_n	
		0	1
D	0	0	1
	1	1	0

$$T = DQ_n' + D'Q_n$$

Logic Diagram(T to D) Flip-Flop Conversion

D:\nQn	0	1
0	0	1
1	1	0

$$T = DQ_n' + D'Q_n$$

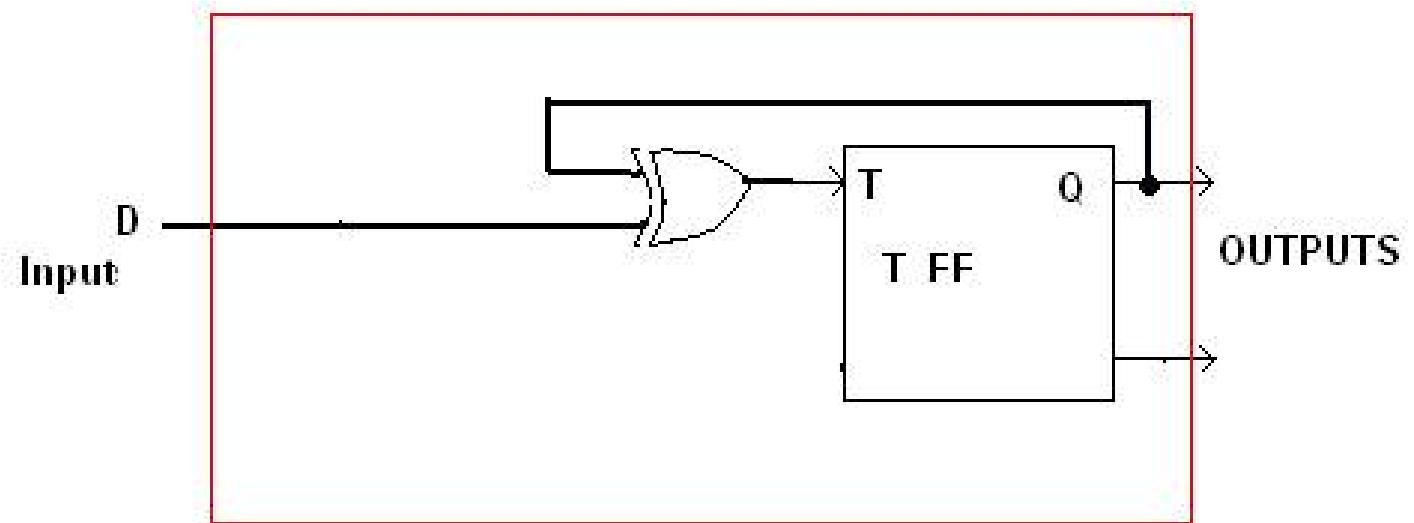

JK(Available) to SR(Target)Flip-flop

Input		Present State	Next State
S	R	Q n	Qn+1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

Flip-flop inputs		Present output	Next output
J	K	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Excitation Table of JK Flip-Flop

Qn	Qn+1	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

JK(Available) to SR(Target)Flip-flop

Conversion Table

Input		Present State	Next State	Flip-Flop Inputs	
S	R	Q n	Qn+1	J	K
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	X	1
1	0	0	1	1	X
1	0	1	1	X	0
1	1	0	X	X	X
1	1	1	X	X	X

JK(Available) to SR(Target) Flip-flop conversion


SR	Qn	
	0	1
00	0	X
01	0	X
11	X	X
10	1	X

$J=S$

SR	Qn	
	0	1
00	X	0
01	X	1
11	X	X
10	0	X

$K=R$

JK to SR Flip-Flop Logic Diagram

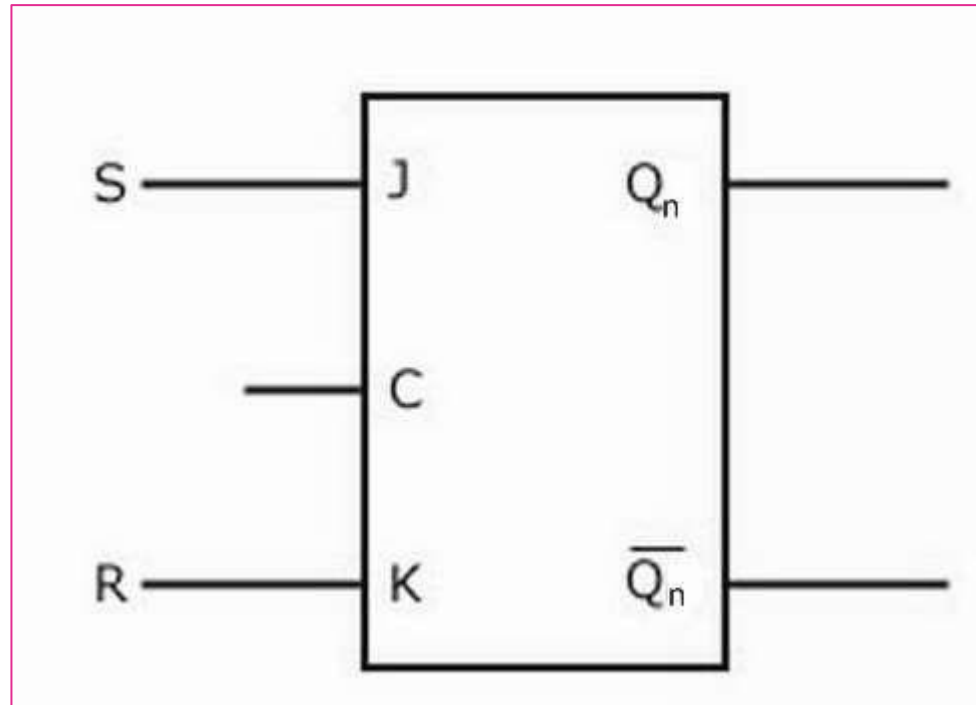

D(Available) to SR(Target) Flip-Flop

Input		Present State	Next State
S	R	Q n	Qn+1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

Excitation Table of D Flip-Flop

Q n	Qn+1	D
0	0	0
0	1	1
1	0	0
1	1	1

D(Available) to SR(Target) Flip-Flop

Conversion Table

Input		Present State	Next State	Flip-Flop Inputs
S	R	Q _n	Q _{n+1}	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	X	x
1	1	1	X	x

D to SR Flip Flop

K- MAP SIMPLIFICATION

		R Qn			
		00	01	11	10
S	0	0	1	0	0
	1	1	1	X	X

$$D = R'Q_n + S$$

Logic Diagram

