




---

# D-JK-T Flip Flop

---


PRESENTED BY NABANITA DAS

# D Flip-Flop

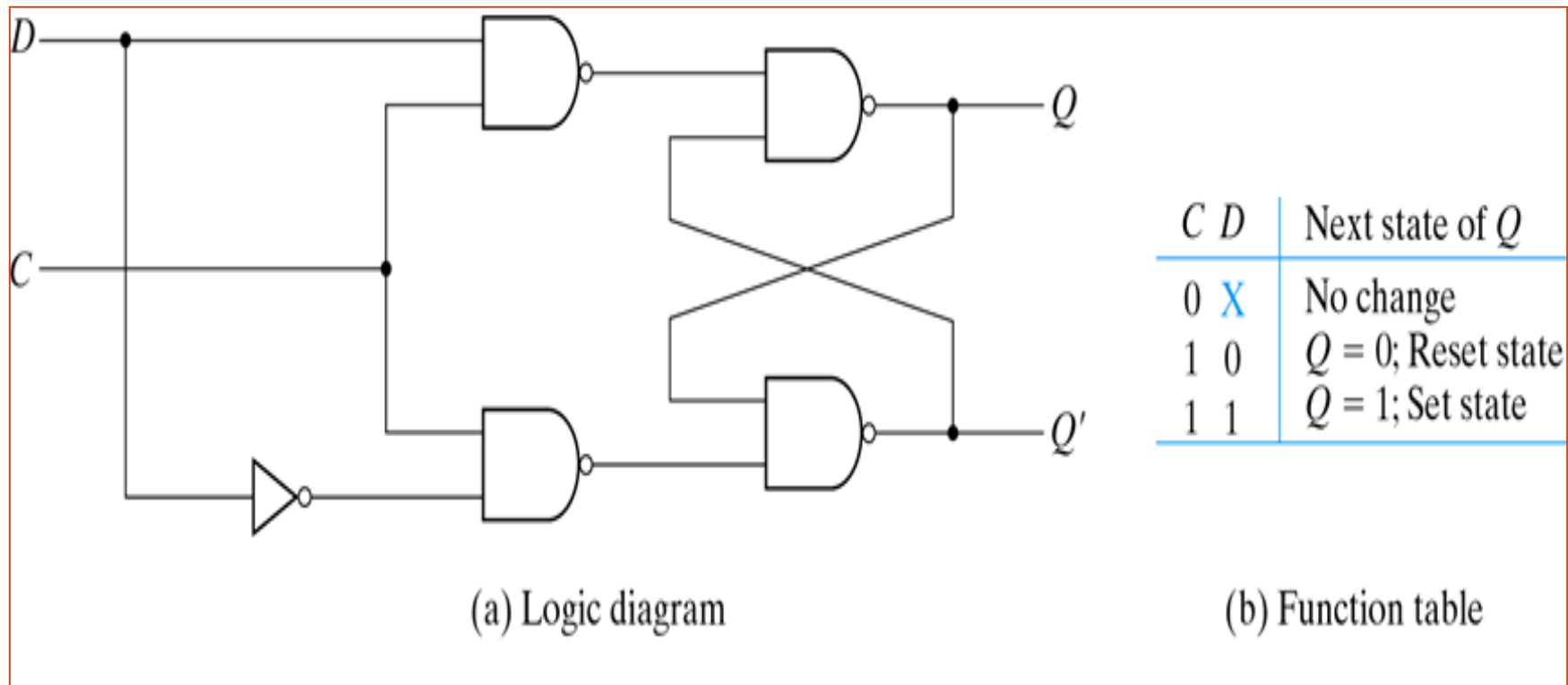


# Timing Diagram of D Flip Flop

---

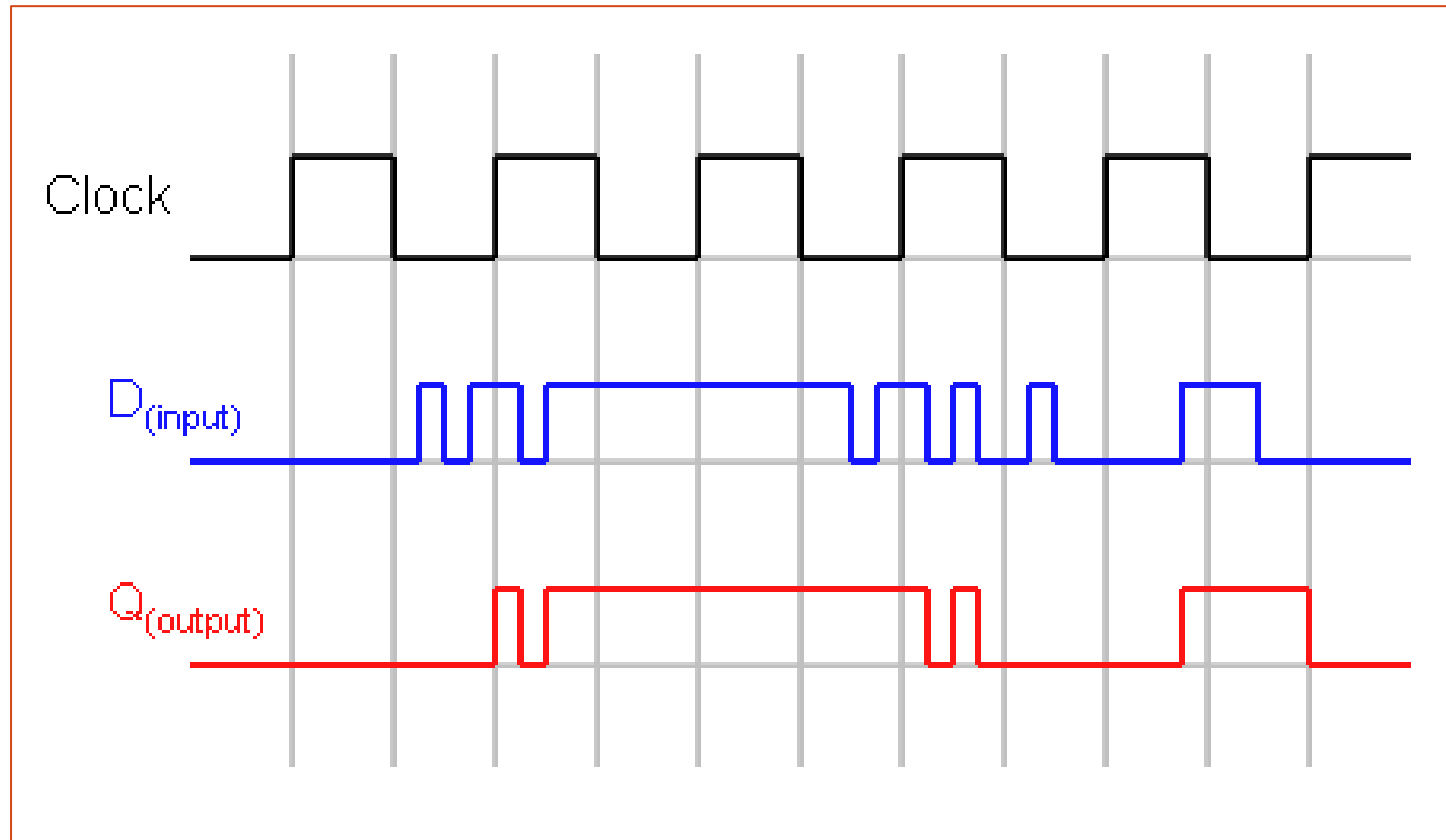

# State Transition Diagram of D Flip Flop

---

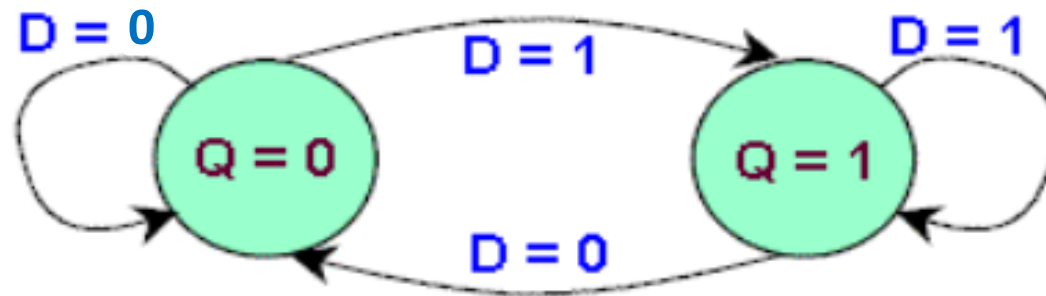


Clk	D	Q	Q'	State
0	0	Q	Q'	No change in state
1	0	0	1	Resets Q to 0
1	1	1	1	Sets Q to 1

# D Flip-Flop

Characteristic Table of an D Flip Flop.

<i>Flip-flop inputs</i>	<i>Present output</i>	<i>Next output</i>
$D$	$Q_n$	$Q_{n+1}$
0	0	0
0	1	0
1	0	1
1	1	1

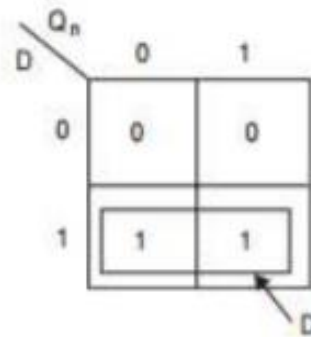Now we will find out the characteristic equation of the D flip-flop from the characteristic table with the help of the Karnaugh map:-





$$Q_{n+1} = D$$

Hence, the characteristic equation of a D flip-flop is
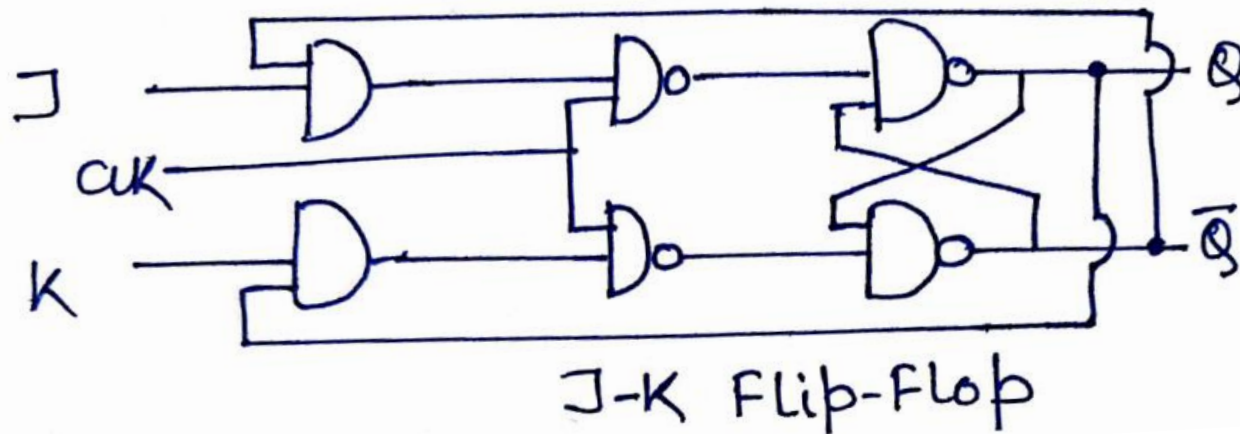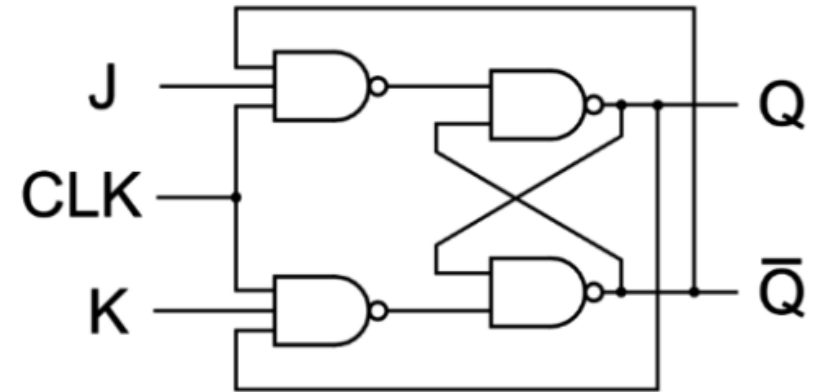
# JK Flip-Flop

JK flip – flop is named after Jack Kilby.


A JK flip – flop is a modification of SR flip – flop. In this the J input is similar to the set input of SR flip – flop and the K input is similar to the reset input of SR flip – flop. The condition  $J = K = 1$  which is not allowed in SR flip – flop ( $S = R = 1$ ) is interpreted as a toggle command.




Clk	J	K	Q	Q'	State
1	0	0	Q	Q'	No change in state
1	0	1	0	1	Resets Q to 0
1	1	0	1	0	Sets Q to 1
1	1	1	-	-	Toggles

# Timing Diagram of JK Flip Flop

---

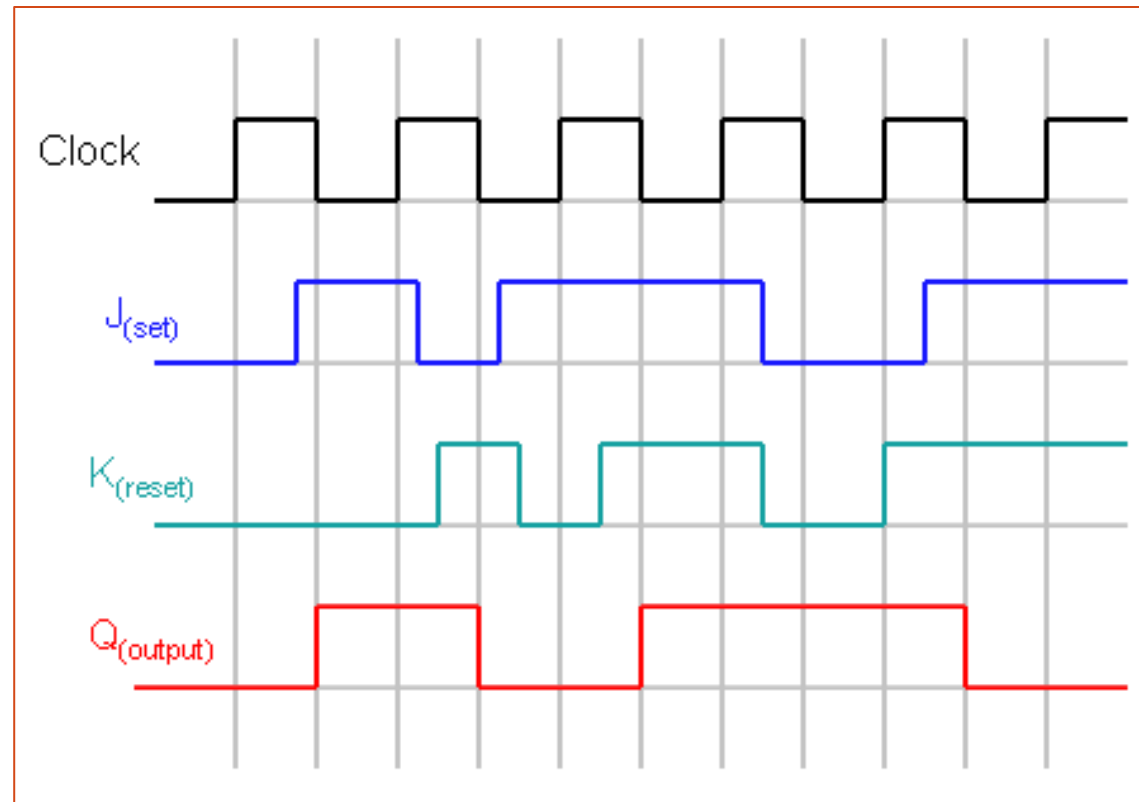
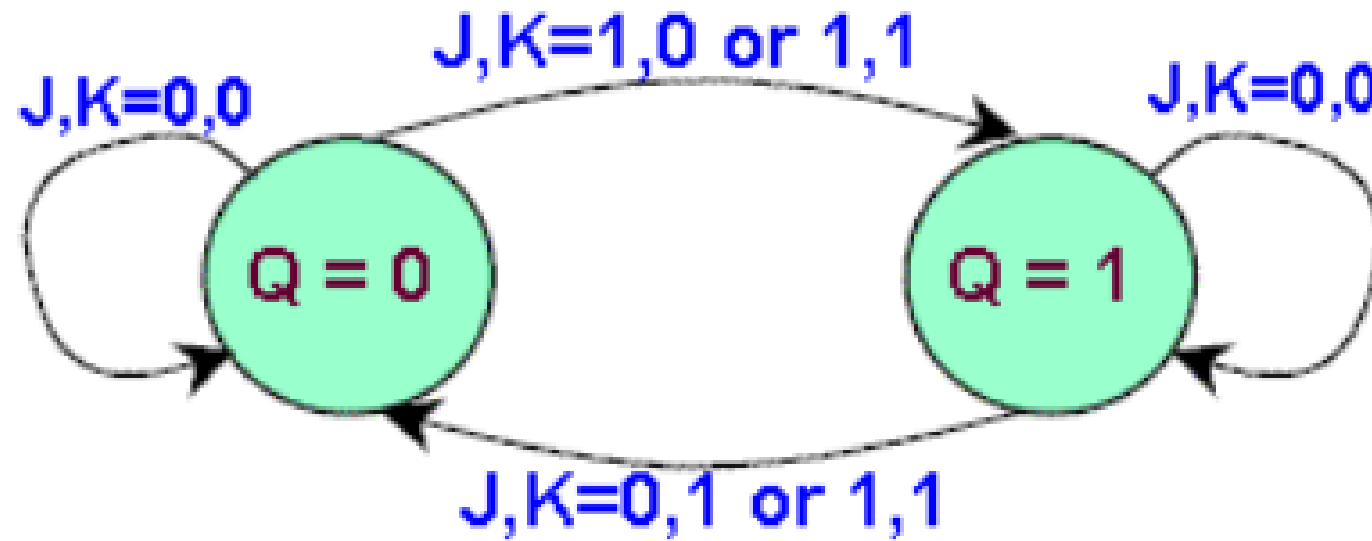
# State Transition Diagram of JK Flip-Flop




Clk	J	K	Q	Q'	State
1	0	0	Q	Q'	No change in state
1	0	1	0	1	Resets Q to 0
1	1	0	1	0	Sets Q to 1
1	1	1	-	-	Toggles



# Characteristic Equation of JK Flip-Flop

As we have already discussed the characteristic equation of an S-R flip-flop, we can similarly find out the characteristic equation of a J-K flip-flop. The characteristic table of a J-K flip-flop is given in the table below. From the characteristic table we have to find out the characteristic equation of the J-K flip-flop.


Flip-flop inputs		Present output	Next output
$J$	$K$	$Q_n$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

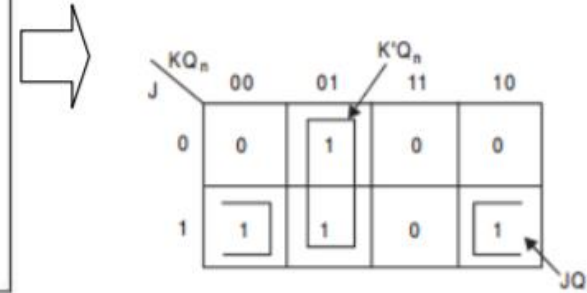

From the Karnaugh map, we obtain  $Q_{n+1} = JQ'_n + K'Q_n$ .  
Hence, the characteristic equation of a J-K flip-flop is

$$Q_{n+1} = JQ'_n + K'Q_n$$


# T (Toggle) flip-flop

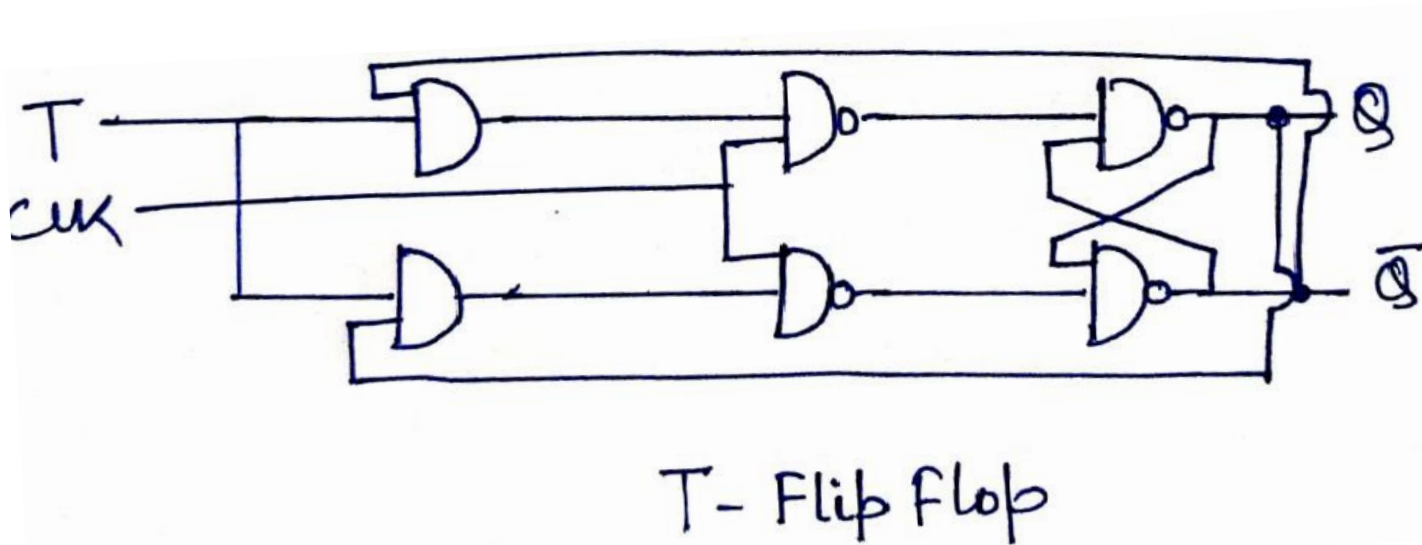

$T$	$Q_n$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

# State Transition Diagram of T Flip-Flop

---

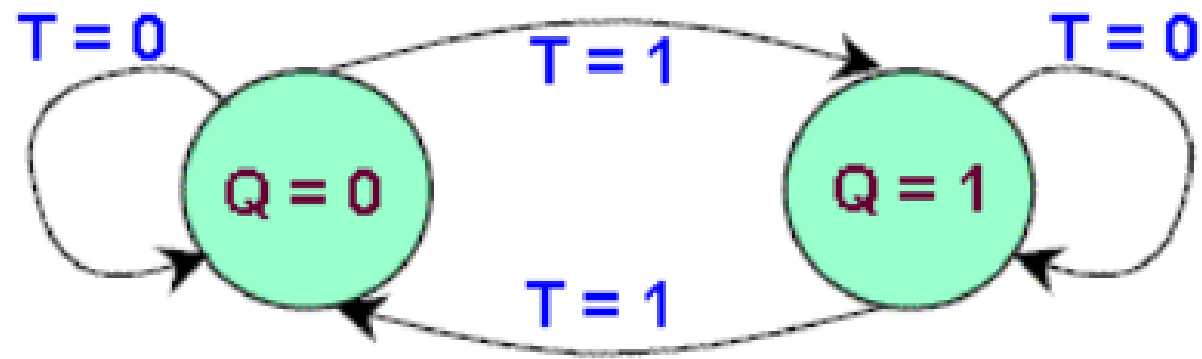

$T$	$Q_n$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

# Characteristic Equation of T Flip-Flop

Now we will find out the characteristic equation of the T flip-flop from the characteristic table with the help of the Karnaugh map below:-

T \ $Q_n$	0	1
0	0	1
1	1	0

<i>Flip-flop inputs</i>	<i>Present output</i>	<i>Next output</i>
$T$	$Q_n$	$Q_{n+1}$
0	0	0
0	1	1
1	0	1
1	1	0

From the Karnaugh map, the Boolean expression of  $Q_{n+1}$  is derived as  $Q_{n+1} = TQ'_n + T'Q_n$ .  
Hence, the characteristic equation of a T flip-flop is

$$Q_{n+1} = TQ'_n + T'Q_n$$